

# **CprE 381 – Computer Organization and Assembly-Level Programming**


## **Lab-03 Report**

Student Name                      Colby McKinley

Section / Lab Time              Section 5 / W 6:10 – 8:00p

*Submit a typeset pdf version of this on Canvas by the due date (i.e., the start of your next lab section). Refer to the highlighted language in the Lab-03 instructions for the context of the following questions.*

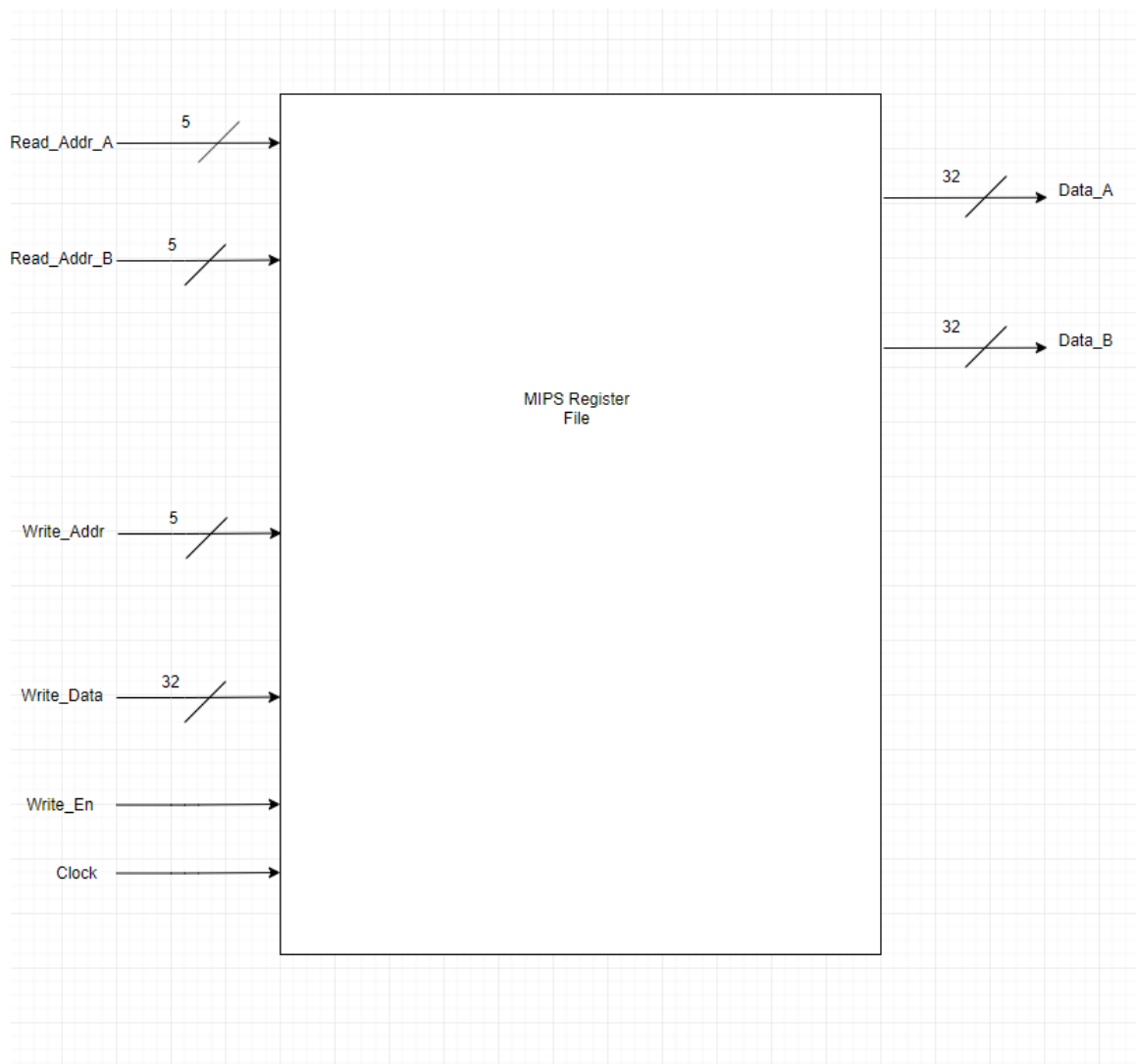- a. [Prelab] At the end of Chapter 5, answer question 5. At the end of Chapter 7, answer exercise 2.  
See /Prelab3.pdf
- b. [Prelab] In your Lab #3 report PDF, provide the Canvas group name for your project team, and a listing of its members. On a scale of 1-10, how comfortable with VHDL does each team member currently feel?  
Group 4  
Colby – 5  
Tyler – 7
- c. [Part 1 (a)] Draw the interface description for the MIPS register file. Which ports do you think are necessary, and how wide (in bits) do they need to be?



- d. [Part 1 (b)] Create an N-bit register using this flip-flop as your basis.
- e. [Part 1 (c)] Waveform.




- f. [Part 1 (d)] What type of decoder would be required by the MIPS register file and why?

In MIPS since there are 32 available registers, a 5 to 32 decoder is required. I will use each read address to as a select line into a decoder to indexing into one of 32 available registers. By making a 5 to 32 decoder, I can use a single 5 bit address bus easier and cleaner, than using single bit many signals for many single bit decoders.


- g. [Part 1 (e)] Waveform.



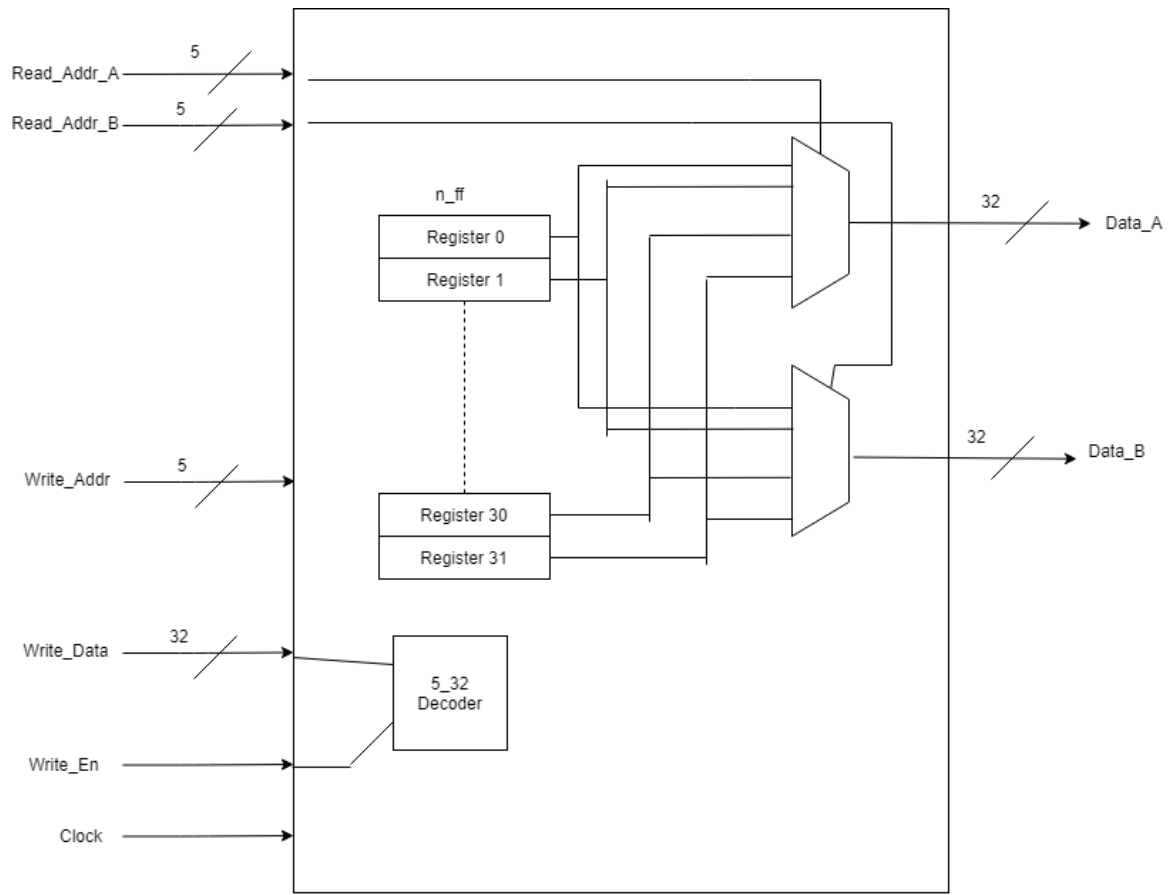


The decoder will be then write enable for each of the registers in the  $n_{ff}$

k. [Part 1 (i)] Waveform.

 

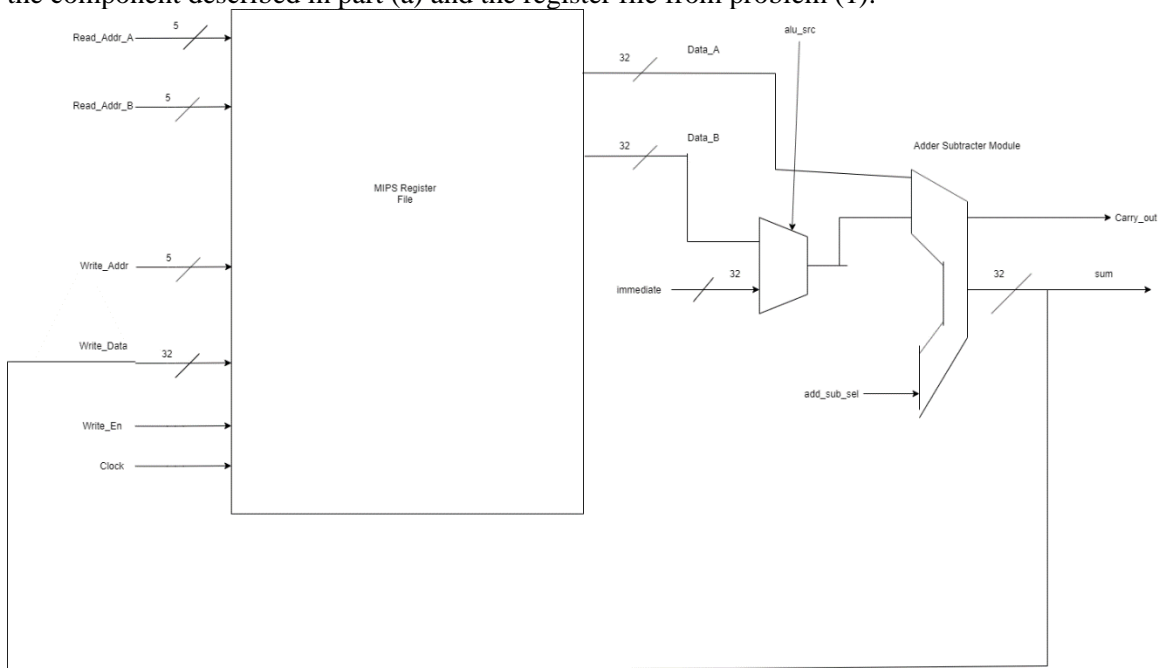1. [Part 2 (b)] Draw a schematic of the simplified MIPS processor datapath consisting only of the component described in part (a) and the register file from problem (1).



- m. [Part 2 (c)] Include in your report waveform screenshots that demonstrate your properly functioning design.

